

Lab 2 report

Name: Oscar Stark Student ID: F11015127

In this lab I implemented a 4x4 adder using 4 full adders and a 4x4 multiplier using 3 4x4 adders.

4x4 adder

4x4 adder code

```
module fourbit_adder(  
    input [3:0] X,  
    input [3:0] Y,  
    input C0,  
    output [3:0] S,  
    output C4  
);  
  
    //3 wires  
    wire C1, C2, C3;  
  
    //4 full adders  
    full_adder FA0 (.X(X[0]), .Y(Y[0]), .C_IN(C0), .C_OUT(C1), .S(S[0]));  
    full_adder FA1 (.X(X[1]), .Y(Y[1]), .C_IN(C1), .C_OUT(C2), .S(S[1]));  
    full_adder FA2 (.X(X[2]), .Y(Y[2]), .C_IN(C2), .C_OUT(C3), .S(S[2]));  
    full_adder FA3 (.X(X[3]), .Y(Y[3]), .C_IN(C3), .C_OUT(C4), .S(S[3]));  
endmodule
```

X and Y are the bits being added, C0 is the carry input, C4 is the carry output and S is the sum. 4 full adders are used.

Test bench

```

module fourbit_adder_sim;

    reg [3:0] X;
    reg [3:0] Y;
    reg CO;
    wire [3:0] S;
    wire C4;


    //Unit under testing
    fourbit_adder uut(.X(X[3:0]), .Y(Y[3:0]), .CO(CO), .S(S[3:0]), .C4(C4));

    //For loops used to test all possible inputs
    integer i, j, k;
    initial begin
        for (i=0; i<16; i=i+1)
            begin
                X=i;
                for (j=0; j<16; j=j+1)
                    begin
                        Y=j;
                        for (k=0; k<2; k=k+1)
                            begin
                                CO=k;
                                #100;
                            end
                        end
                    end
            end
        end
    endmodule

```

All possible inputs are simulated.

Simulation results

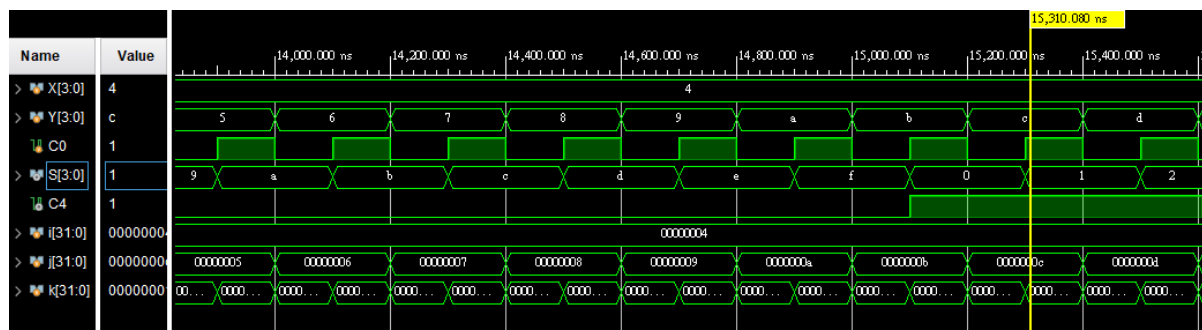

X, Y and C0 are the inputs. S and C4 are the outputs.

4x4 multiplier

4x4 multiplier code

```
module fourbitmultiplier(  
    input [3:0] X,  
    input [3:0] Y,  
    output [7:0] P  
);  
  
    //array with 16 and gates  
    wire [15:0] A;  
    and(A[0], X[0], Y[0]);  
    and(A[1], X[1], Y[0]);  
    and(A[2], X[2], Y[0]);  
    and(A[3], X[3], Y[0]);  
    and(A[4], X[0], Y[1]);  
    and(A[5], X[1], Y[1]);  
    and(A[6], X[2], Y[1]);  
    and(A[7], X[3], Y[1]);  
    and(A[8], X[0], Y[2]);  
    and(A[9], X[1], Y[2]);  
    and(A[10], X[2], Y[2]);  
    and(A[11], X[3], Y[2]);  
    and(A[12], X[0], Y[3]);  
    and(A[13], X[1], Y[3]);  
    and(A[14], X[2], Y[3]);  
    and(A[15], X[3], Y[3]);
```

```

//arrays with the input for the first FBA
wire [3:0] X1;
assign X1[2:0] = A[3:1];
assign X1[3]=0;
wire [3:0] Y1;
assign Y1[3:0] = A[7:4];
wire [3:0] S1;
wire C_OUT1;
//first FBA
fourbit_adder FBA1 (.X(X1[3:0]), .Y(Y1[3:0]), .CO(0), .C4(C_OUT1), .S(S1));

//arrays with the input for the second FBA
wire [3:0] X2;
assign X2[2:0] = S1[3:1];
assign X2[3] = C_OUT1;
wire [3:0] Y2;
assign Y2[3:0] = A[11:8];
wire [3:0] S2;
wire C_OUT2;
//second FBA
fourbit_adder FBA2 (.X(X2[3:0]), .Y(Y2[3:0]), .CO(0), .C4(C_OUT2), .S(S2));

//arrays with the input for the third FBA
wire [3:0] X3;
assign X3[2:0] = S2[3:1];
assign X3[3] = C_OUT2;
wire [3:0] Y3;
assign Y3[3:0] = A[15:12];
wire [3:0] S3;
wire C_OUT3;
//third FBA
fourbit_adder FBA3 (.X(X3[3:0]), .Y(Y3[3:0]), .CO(0), .C4(C_OUT3), .S(S3));

//P is an array with the result of the multiplication
wire [7:0] P;
assign P[0] = A[0];
assign P[1] = S1[0];
assign P[2] = S2[0];
assign P[6:3] = S3[3:0];
assign P[7] = C_OUT3;
endmodule

```

X and Y are the factors, P is the product. The results of 16 and gates are stored in the array A. 3 four bit adders are used.

Test bench

```

module fourbitmultiplier_sim;
    reg [3:0] X;
    reg [3:0] Y;
    wire [7:0] P;



    //Unit under test
    fourbitmultiplier uut(.X(X[3:0]), .Y(Y[3:0]), .P(P[7:0]));

    //For loops used to test all possible inputs
    integer i, j;
    initial begin
        for (i=0; i<16; i=i+1)
            begin
                X=i;
                for (j=0; j<16; j=j+1)
                    begin
                        Y=j;
                        #100;
                    end
            end
        end
    endmodule

```

All possible inputs are simulated.

Simulation results

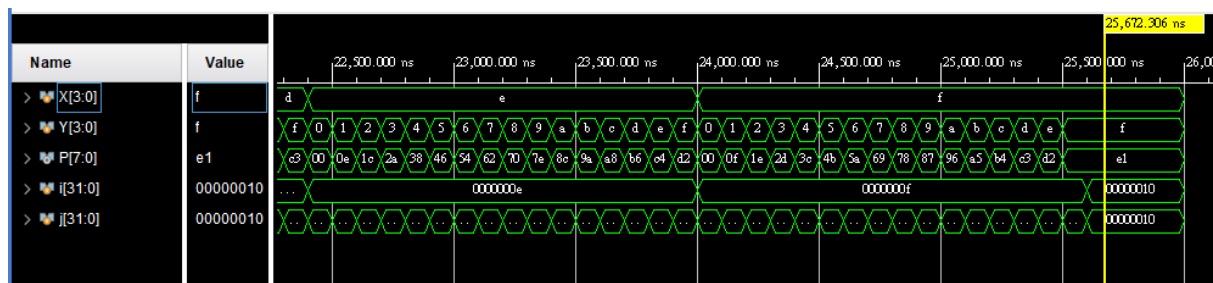 

X, Y are the inputs. P is the output.