

Lab 1 report

Name: Oscar Stark Student ID: F11015127

In this lab I implemented a half adder and a full adder.


Half adder

Half adder code

```
module half_adder(  
    input X,  
    input Y,  
    output C,  
    output S  
);  
    wire X, Y, C, S;  
    xor(S, X, Y);  
    and(C, X, Y);  
endmodule
```

X and Y are the bits being added, C is the carry and S is the sum.

Schematic

 


The half adder uses 1 AND gate and 1 XOR gate.

Test bench

```
module half_adder_sim;
    reg X, Y;
    wire C, S;
    half_adder uut(.X(X), .Y(Y), .C(C), .S(S));
    initial begin
        X=0;Y=0;
        #100;
        X=0;Y=1;
        #100;
        X=1;Y=0;
        #100;
        X=1;Y=1;
        #100;
    end
endmodule
```

All possible inputs are simulated.

Simulation results

 

X and Y are the bits being added, C is the carry and S is the sum.


Full adder

Full adder code

```
) module full_adder(  
    input X,  
    input Y,  
    input C_IN,  
    output C_OUT,  
    output S,  
    output S1,  
    output C1,  
    output C2,  
    output C3  
);  
wire X, Y, C_IN, C_OUT, S, S1, C1, C2, C3;  
  
xor(S1, X, Y);  
xor(S, S1, C_IN);  
  
and(C1, X, Y);  
and(C2, X, C_IN);  
and(C3, Y, C_IN);  
or(C_OUT, C1, C2, C3);  
) endmodule
```

X and Y are the bits being added, C_IN is the carry input, C_OUT is the carry output and S is the sum. S1, C1, C2, C3 are just wires.

Schematic

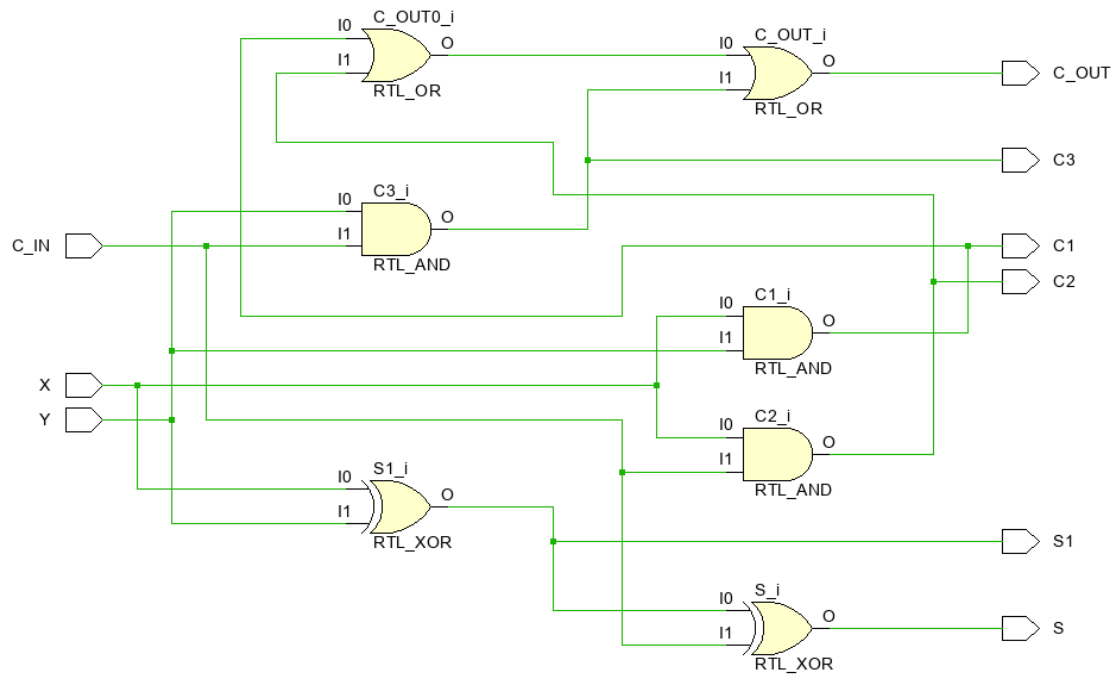


The circuit has 3 AND gates, 2 XOR gates and 2 OR gates.

Test bench

```
module full_adder_sim2;  
    reg X, Y, C_IN;  
    wire S, C_OUT;  
    full_adder uut(.X(X), .Y(Y), .C_IN(C_IN), .S(S), .C_OUT(C_OUT));  
    initial begin  
        X=0;Y=0;C_IN=0;  
        #100;  
        X=0;Y=0;C_IN=1;  
        #100;  
        X=0;Y=1;C_IN=0;  
        #100;  
        X=0;Y=1;C_IN=1;  
        #100;  
        X=1;Y=0;C_IN=0;  
        #100;  
        X=1;Y=0;C_IN=1;  
        #100;  
        X=1;Y=1;C_IN=0;  
        #100;  
        X=1;Y=1;C_IN=1;  
        #100;  
    end  
endmodule
```

All possible inputs are simulated.

Simulation results

 

X, Y and C_IN are the inputs. S and C_OUT are the outputs.