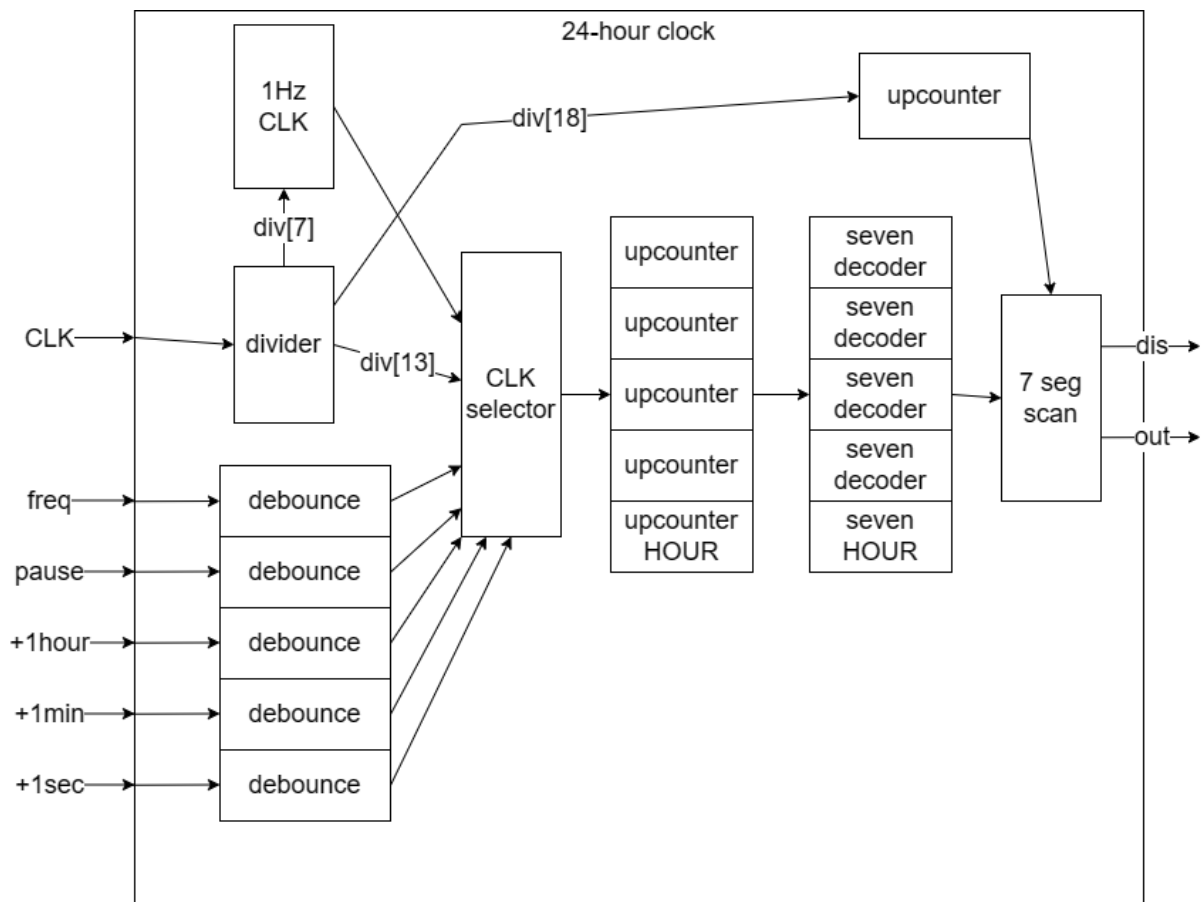


# Lab 6 report

Name: Oscar Stark Student ID: F11015127

In this lab I implemented a 24-hour clock displayed in seven segments with a reset button. Only the code for the advanced task is shown on this report, because the advanced is just an extension of the basic task.

## Circuit block diagram



# Verilog code

## Main code

```
module task1(CLK, BplusSec, BplusMin, BplusHour, OUTleft, OUTright, DIS, Spause, Sfreq, reset);
    input CLK, BplusSec, BplusMin, BplusHour, Spause, Sfreq, reset;
    output reg [6:0] OUTleft, OUTright; //for the 4 7SD on the left and the 4 on the right
    output reg [5:0] DIS; //to choose which 7SD lights up

    //wires
    wire [31:0] DIV;
    wire BplusSec_CLK, BplusMin_CLK, BplusHour_CLK, Spause_CLK, Sfreq_CLK;
    wire [3:0] BCD1, BCD2, BCD3, BCD4, HOUR;
    wire [6:0] OUT1, OUT2, OUT3, OUT4, OUT5;
    wire [13:0] OUT56; //this out is different because it's for the hours
    wire [4:0] hour;
    wire C1, C2, C3, C4;
    wire CLK_1Hz;
    //registers
    reg CLK_sec, CLK_min, CLK_hour;

    divider DIVIDER(CLK, DIV, reset);
    debounce Dsec(DIV[16], BplusSec, BplusSec_CLK, reset);
    debounce Dmin(DIV[16], BplusMin, BplusMin_CLK, reset);
    debounce Dhour(DIV[16], BplusHour, BplusHour_CLK, reset);
    debounce Dpause(DIV[16], Spause, Spause_CLK, reset);
    debounce Dfreq(DIV[16], Sfreq, Sfreq_CLK, reset);

    //1Hz Clock. DIV[7]*390625 = 1s
    upcounter1Hz(DIV[7], reset, 390624, CLK_1Hz);
```

```

//Clock selector
always@(CLK)
begin
    if(Spause_CLK)//if the 24h clock is paused,
    begin        //the buttons can be used to adjust the time
        CLK_sec <= BplusSec_CLK;
        CLK_min <= BplusMin_CLK;
        CLK_hour <= BplusHour_CLK;
    end
    else
    begin        //if the 24h clock is not paused,
        if(Sfreq_CLK)//a switch is used to choose the frequency
            CLK_sec <= DIV[13];
        else
            CLK_sec <= CLK_1Hz;
        CLK_min <= C2;
        CLK_hour <= C4;
    end
end

/////////////////////////////////////////////////////////////////
//2 upcounters for the seconds, 2 upcounters for the minutes,
//and 1 upcounterHOURL for the hours
upcounter UPC1(CLK_sec, BCD1, reset, 5, 9, C1, 0);
upcounter UPC2(C1, BCD2, reset, 4, 5, C2, Spause_CLK);
upcounter UPC3(CLK_min, BCD3, reset, 9, 9, C3, 0);
upcounter UPC4(C3, BCD4, reset, 5, 5, C4, Spause_CLK);
upcounterHOURL UPC56(CLK_hour, HOUR, reset, 23, 23);

/////////////////////////////////////////////////////////////////.
//2 seven decoders for the seconds, 2 seven decoders for the minutes,
//and 1 sevenHOURL for the hours
seven SEV1(BCD1, OUT1);
seven SEV2(BCD2, OUT2);
seven SEV3(BCD3, OUT3);
seven SEV4(BCD4, OUT4);
sevenHOURL SEV56(HOUR, OUT56);

```

```

//seven seg scan
wire [3:0] DIScounter;//every DIV[18] the display lit up changes
upcounter DISupc(DIV[18], DIScounter, reset, 0, 2);
always@(DIScounter)
begin
    if(DIScounter==0)
    begin
        OUTright <= OUT1;
        OUTleft <= OUT4;
        DIS <= 6'b001001;
    end
    else
    if(DIScounter==1)
    begin
        OUTright <= OUT2;
        OUTleft <= OUT56[6:0];
        DIS <= 6'b010010;
    end
    else
    if(DIScounter==2)
    begin
        OUTright <= OUT3;
        OUTleft <= OUT56[13:7];
        DIS <= 6'b100100;
    end
end
endmodule

```

## Divider

```

module divider(CLK, DIV, reset);
    input CLK, reset;
    output reg [31:0] DIV;

    always @(posedge CLK, posedge reset)
    begin
        if(reset)
            DIV <= 0; //reset button sets DIV to 0
        else
            DIV <= DIV+1; //posedge CLK adds 1 to the DIV
    end
endmodule

```

## D Flip Flop

```
module DFF(CLK, D, Q, reset);
    input CLK, D, reset;
    output reg Q;

    always @(posedge CLK, posedge reset)
    begin
        if(reset)    Q <= 1'b0; //reset button sets Q to 0
        else        Q <= D; //CLK sets Q = D
    end
endmodule
```

---

## Debounce

```
module debounce(CLK, BUTTON, BUTTON_CLK, reset);
    input CLK, BUTTON, reset;
    output reg BUTTON_CLK;

    wire[2:0] W;

    //3 D Flip Flops
    DFF DFF1(CLK, BUTTON, W[0], reset);
    DFF DFF2(CLK, W[0], W[1], reset);
    DFF DFF3(CLK, W[1], W[2], reset);

    always@(W)
        BUTTON_CLK <= W[0] & W[1] & W[2];

endmodule
```

---

## 1Hz clock

```
//upcounter modified to work as a 1Hz clock
} module upcounter1Hz(CLK, reset, max, carry);
    input CLK, reset;
    input [18:0] max;
    output reg carry;
    reg [18:0] oneHz;
} always @(posedge CLK, posedge reset)
} begin
}     if(reset)
}     begin
        oneHz <= 0;
        carry <= 0;
}     end
}     else
}     if(oneHz==max)
}     begin
        oneHz <= 0;
        carry <= 1;
}     end
}     else
}     begin
        oneHz <= oneHz+1;
        carry <= 0;
}     end
}     end
} endmodule
```

## Up counter

```
//the upcounter has a lot of arguments so it can be used in many
//different ways
module upcounter(CLK, BCD, reset, resetvalue, max, carry, carrycontrol);
    input CLK, reset, carrycontrol;
    input [3:0] resetvalue;
    input [3:0] max;
    output reg [3:0] BCD;
    output reg carry;

    always @(posedge CLK, posedge reset)
    begin
        if(reset)
        begin
            BCD <= resetvalue;
            carry <= 0;
        end
        else
        if(BCD==max)//max is the maximum digit
        begin
            BCD <= 0;
            if(carrycontrol==0)//carrycontrol is used to stop the carry
                carry <= 1;    //from being set to 1 while adjusting the time
        end
        else
        begin
            BCD <= BCD+1;
            carry <= 0;
        end
    end
endmodule
```

## Hour up counter

```
//upcounter modified to represent the hours
module upcounterHOUR(CLK, HOUR, reset, resetvalue, max);
    input CLK, reset;
    input [4:0] resetvalue;
    input [4:0] max;
    output reg [4:0] HOUR;

    always @(posedge CLK, posedge reset)
    begin
        if(reset)
        begin
            HOUR <= resetvalue;
        end
        else
        begin
            if(HOUR==max)
            begin
                HOUR <= 0;
            end
            else
            begin
                HOUR <= HOUR+1;
            end
        end
    end
endmodule
```

## Seven segment decoder



```

module seven(BCD, OUT);
    input [3:0] BCD; //the input in BCD
    output reg [6:0] OUT; //the out put for the 7SD

    always@(BCD) // this controls how the 7SD lights up
    case({BCD})
        4'b0000: {OUT} = 7'b1111110; // 0
        4'b0001: {OUT} = 7'b0110000; // 1
        4'b0010: {OUT} = 7'b1101101; // 2
        4'b0011: {OUT} = 7'b1111001; // 3
        4'b0100: {OUT} = 7'b0110011; // 4
        4'b0101: {OUT} = 7'b1011011; // 5
        4'b0110: {OUT} = 7'b1011111; // 6
        4'b0111: {OUT} = 7'b1110000; // 7
        4'b1000: {OUT} = 7'b1111111; // 8
        4'b1001: {OUT} = 7'b1111011; // 9
    endcase
endmodule

```


## Hour seven segment decoder

```
//seven decoder modified to represent the hours
) module sevenHOUR(HOUR, OUT);
    input [4:0] HOUR;
    output reg [13:0] OUT;


)    always@(HOUR) // this controls how the 7SD lights up
)        case({HOUR})
            5'b00000: {OUT} = 14'b11111101111110; // 0
            5'b00001: {OUT} = 14'b11111100110000; // 1
            5'b00010: {OUT} = 14'b11111101101101; // 2
            5'b00011: {OUT} = 14'b11111101111001; // 3
            5'b00100: {OUT} = 14'b11111100110011; // 4
            5'b00101: {OUT} = 14'b11111101011011; // 5
            5'b00110: {OUT} = 14'b11111101011111; // 6
            5'b00111: {OUT} = 14'b11111101100000; // 7
            5'b01000: {OUT} = 14'b11111101111111; // 8
            5'b01001: {OUT} = 14'b11111101111011; // 9
            5'b01010: {OUT} = 14'b01100001111110; // 10
            5'b01011: {OUT} = 14'b01100000110000; // 11
            5'b01100: {OUT} = 14'b01100001101101; // 12
            5'b01101: {OUT} = 14'b01100001111001; // 13
            5'b01110: {OUT} = 14'b01100000110011; // 14
            5'b01111: {OUT} = 14'b01100001011011; // 15
            5'b10000: {OUT} = 14'b01100001011111; // 16
            5'b10001: {OUT} = 14'b01100001110000; // 17
            5'b10010: {OUT} = 14'b01100001111111; // 18
            5'b10011: {OUT} = 14'b01100001111011; // 19
            5'b10100: {OUT} = 14'b11011011111110; // 20
            5'b10101: {OUT} = 14'b11011010110000; // 21
            5'b10110: {OUT} = 14'b11011011101101; // 22
            5'b10111: {OUT} = 14'b11011011111001; // 23
        endcase
) endmodule
```

---

## FPGA board results

 

 The time is 23:59:45. The clock resets to this time.



The time is 3:19:37.